

NAME: SATVIK SHRIVASTAVA


ROLL No.: 2003131


CS221 ASSIGNMENT

TASK 1

1. Plot the graph, area in LUT slices (vs) No. of registers (NREG) as well as delay (vs) No. of registers (NREG) for the register file module for NREG = 16, 32, 64. Set DSIZE (bit-width of each register) =32.

No. of Registers (NREG)	Bit-width of the register (DSIZE)	No of register slices used	No of LUT slices used	Minimum clock Period in ns
4	32	128/106400	186/53200	3.602
8	32	256/106400	302/53200	4.003
16	32	512/106400	502/53200	4.402
32	32	1024/106400	900/53200	6.11
64	32	1024/106400	900/53200	7.47

 


 


2) Plot the graph, area in LUT slices (vs) bit-width of register (DSIZE) as well as delay (vs) bit-width of register (DSIZE) for the register file module for DSIZE = 16, 32, 64. Set NREG (number of registers) =32.

Bit-width of the register (DSIZE)	No. of registers (NREG)	No of register slices used	No of LUT slices used	minimum clock period in ns
4	32	128/106400	144/53200	6.07
8	32	256/106400	252/53200	6.097
16	32	512/106400	468/53200	6.339
32	32	1024/106400	900/53200	6.38
64	32	2048/106400	1764/53200	(Some error was occuring) *

 LUT slices (vs) bit-width of register (DSIZE)



Delay (vs) bit- width of register

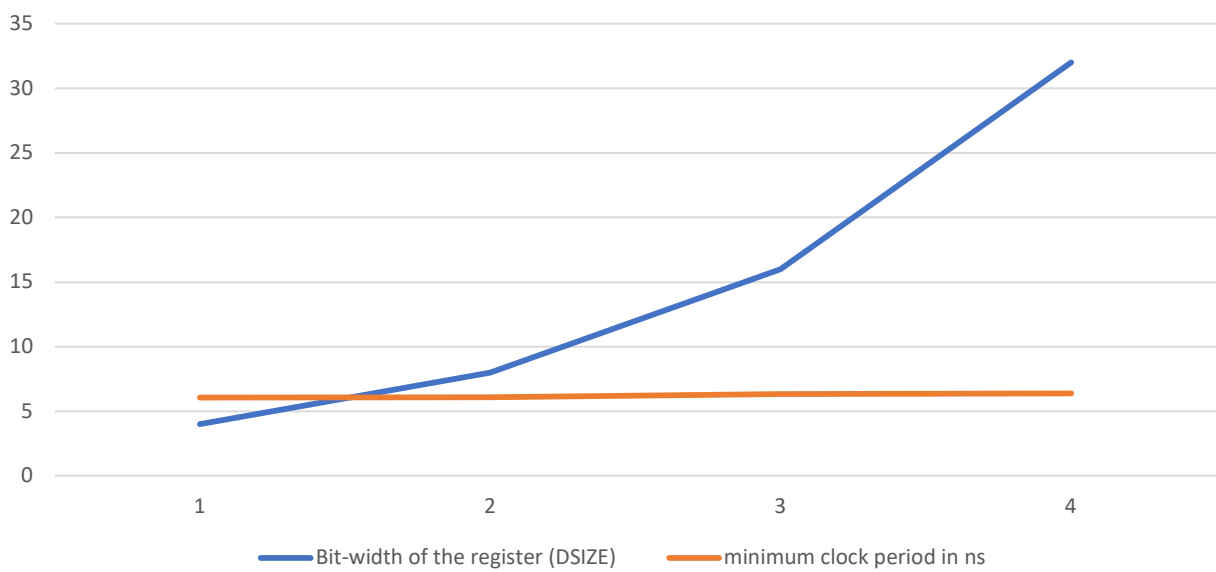

TASK 2

You need to set the input bit-width to 8, 16 and 32 (one by one) and find out the number of slices used. You need to plot area (vs) bit-width as well as delay (vs) bit-width for the ALU module. In FPGA you cannot find area directly so instead of area you can take number of slices, which would be considered proportional to the area.

Bit-width of the register (DSIZE)	No. of registers (NREG)	No of LUT slices used/53200	minimum clock period in ns
8	32	8	8.438
16	32	16	8.416
32	32	32	11.037

